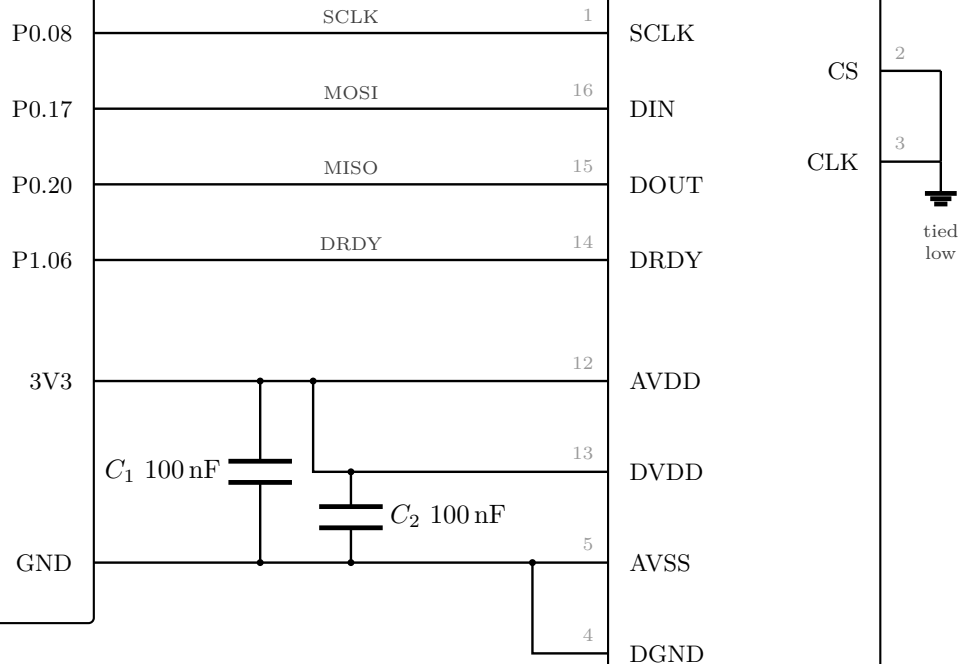



nice!nano

ADS1220



digital & power view — SPI mode 1; CS and CLK tied to GND (internal oscillator; no `cs-gpios` in devicetree);
 C_1 on AVDD, C_2 on DVDD (100 nF each); analog pins in figure 2

ADS1220

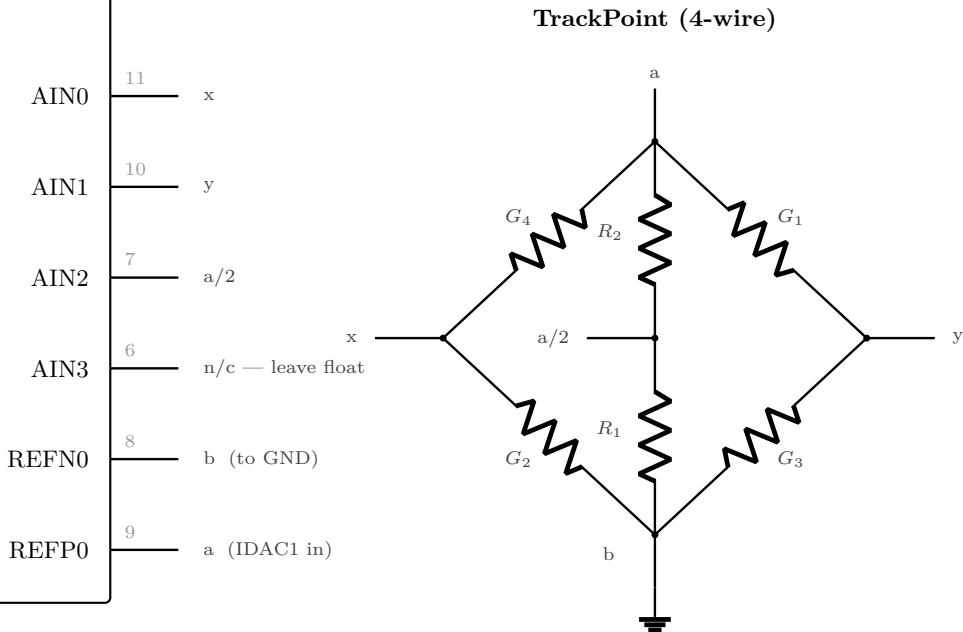

symbols join by matching labels. Two half-bridges share a/b ; x, y = taps; AIN3 must float.

Excitation IDAC1 enters at **a**, returns via **b** to GND. $R_1 = R_2 = 10\text{ k}$ matched $\Rightarrow$ AIN2 = $a/2 \Rightarrow$ differential input ≈ 0 at rest.