
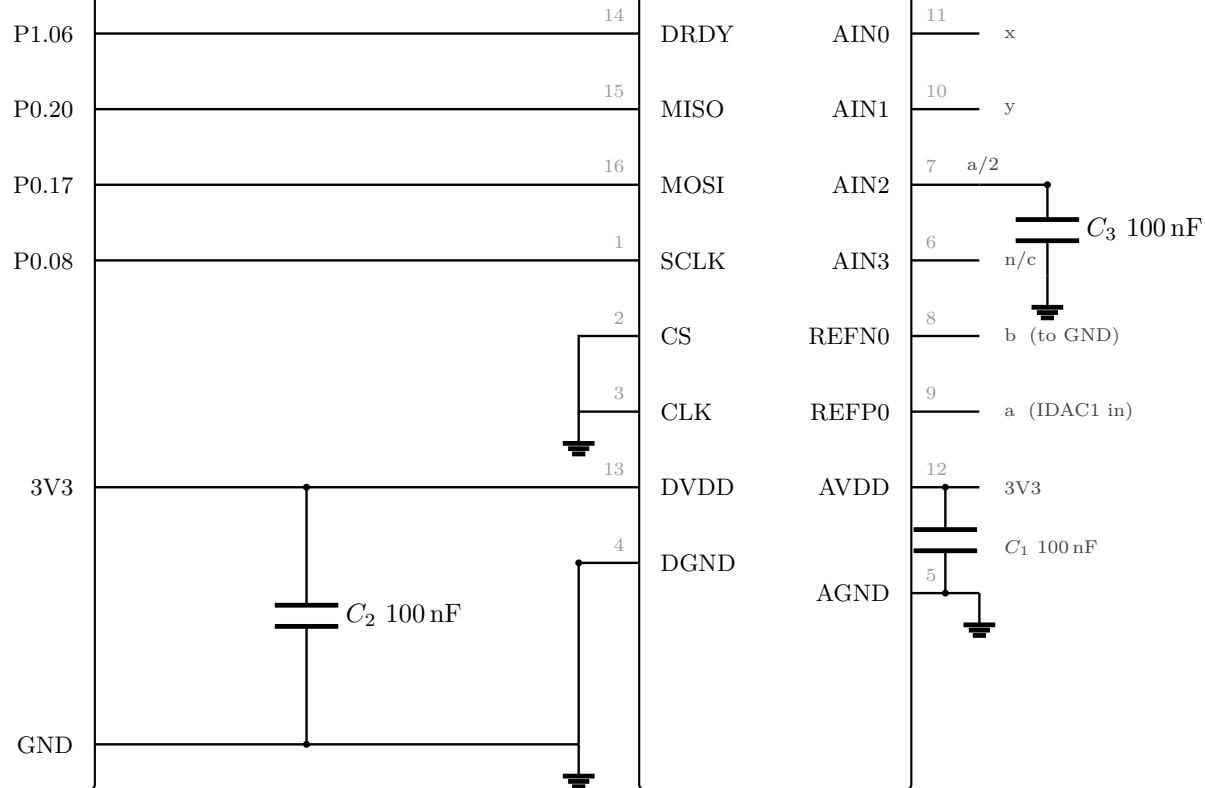


nice!nano

ADS1220

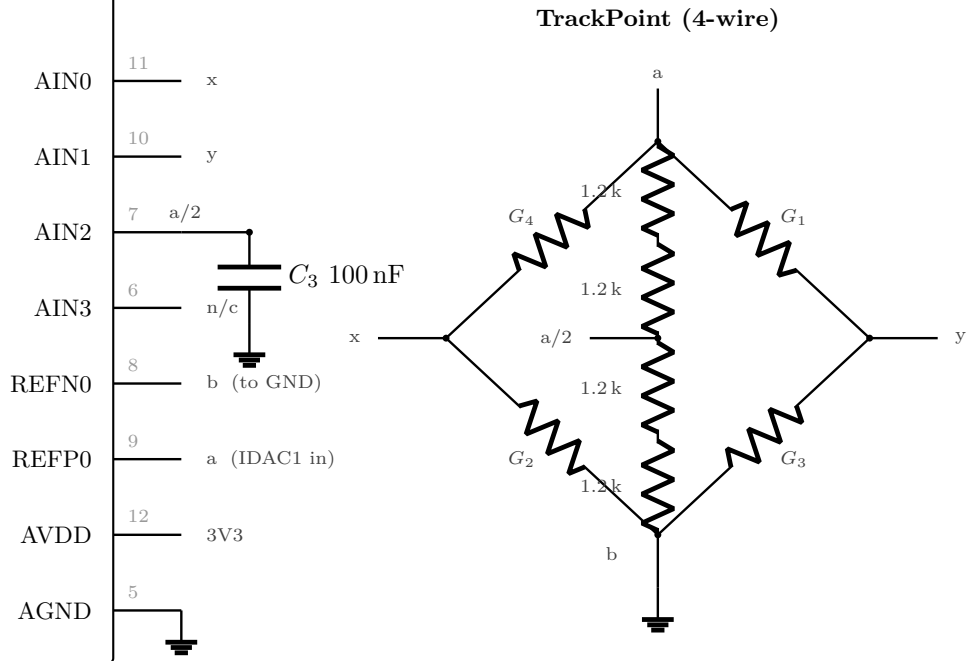

ADS1220



right-side pins in module order; left column (DRDY ... DGND) in figure 1. Symbols join by matching labels. Two half-bridges share a/b; x, y = taps; AIN3 must float. Excitation IDAC1 enters at a, returns via b to GND.

$R_2 = R_1 = 2 \times 1.2 \text{ k} = 2.4 \text{ k}$ matched $\Rightarrow$ AIN2 = a/2; $C_3 = 100 \text{ nF}$ at AIN2 $\Rightarrow$ differential input ≈ 0 at rest.